

Answer ALL Questions

I-a) A sequential circuit has one J-K flip flop with output A and one D-flip flop with output B, one input Y, and one output Z. The flip flops and output equations are as follows:

$$J_A = BY + \bar{B} \quad , \quad K_A = \bar{B}Y \quad , \quad D_B = \bar{A}Y \quad , \quad Z = AY + B\bar{Y}$$

i- Draw the logic diagram of the circuit, ii- Derive the state table, iii- Draw the state diagram.

b) Given the state diagram shown in Fig.1, design and implement the corresponding sequential circuit using J-K flip flops.

II-a) Excess-3 code is generated by adding 3 to the BCD code. State a truth table showing the decimal digits 1, 2, 3,.....9, the corresponding BCD code, and the corresponding excess-3 code.

i- Design a combinational logic circuit that converts a 4-bit BCD input to its corresponding 4-bit excess-3 output. Implement your design using discrete AND, OR, XOR, and INVERTER gates.

ii- Implement the BCD-to-Excess-3 code converter in part (i) using programmable logic array (PLA) with 4-inputs and 4-outputs.

b) A BCD-to-Seven segment decoder is a combinational circuit that accepts a decimal digit in BCD and generates the appropriate outputs for selection of segments in a display indicator displaying the decimal digit as shown in Fig.2. State a truth table for BCD-to-Seven segment decoder. Design and implement the corresponding combinational circuit using:

i- A 16x7 ROM

ii- A programmable array logic (PAL) consisting of 4-inputs, 7-outputs, 7-sections each consisting of four-wide AND-OR array. One of the outputs is feed back to input.

III-a) Derive the synchronous input equations of a 4-bit synchronous binary counter based on D-type flip flops. Draw the corresponding counter circuit with the provision of Count Enable connection.

b) Design a combinational circuit that compares two 4-bit numbers A and B to check if they are equal. The circuit has one output Y so that Y=1 if A=B and Y=0 if A is not equal to B. Implement your design using discrete logic gates.

IV-a) Some microprocessors do not provide a separate address bus, instead they use the data bus for address transmission by multiplexing. With the aid of graphical illustration explain the multiplexed bus configuration system.

b) In a certain μP , the main program runs from address D110 to D193. Four nested subroutines have their start and end addresses as:

subroutine A \rightarrow A200 to A235

subroutine B \rightarrow A239 to A258

subroutine C \rightarrow C1A1 to C1A9

subroutine D \rightarrow C239 to C258

The BRANCH instructions are at the following addresses:

subroutine A \rightarrow D122

subroutine B \rightarrow A232

subroutine C \rightarrow A249

 


Fig. 1

 


Fig. 2

اقاب الصفحة من فضلك

subroutine D → C1A4

i-If the CPU internal stack registers are used, graphically show what the stack registers will contain after each push and pop operation.

ii-If a memory type stack whose addresses run from B138 to B13D (6-deep stack) is used.

Graphically show the contents of the stack, the stack pointer, and program counter after all branches and returns for all four subroutines.

V-a) In a certain μP the effective addresses of some locations in data memory are pre-stored in scratch pad locations as follows:

| Memory address | Scratch pad address |
|----------------|---------------------|
| 112B | 02 |
| 13AC | 03 |
| 146E | 04 |
| 003A | 05 |
| 003B | 06 |
| 003C | 07 |

The data for operands A, B, and C are stored in the locations: A in location 112B, B in location 13AC, and C in location 146E. Write a program using the codes given in the tables attached to first clear the accumulator, then perform the following operations using the previously cleared accumulator and Indirect addressing Mode:

1. $A+B=W$, and W to be stored in the memory location 003A
2. $W-C=X$, and X to be stored in the memory location 003B
3. $X+W=Z$, and Z to be stored in the memory location 003C

b) The accumulator of a certain μP contains 35_H . The location to be accessed in the data memory contains 54_H . The instruction which uses the program counter relative addressing mode, is fetched from address 0554_H of the program memory. The A field of the instruction contains 81_H . The O field of the instruction commands the μP to transfer the contents of the accessed data memory location into the accumulator and add it to the previous contents.

i- Determine the contents of instruction register, the program counter after the instruction is fetched, the MAR, and the accumulator after the instruction is executed.

ii- If the programmer by mistake inserted 71_H in the A field of the instruction instead of 81_H . Repeat part (i) showing the effect of this error.

GOOD LUCK

Table 5-3 THE M-FIELD CODES FOR THE GEMINI-A INSTRUCTIONS

| Binary | HEX | Instructions |
|--------|-----|---|
| 0000 | 0 | Direct addressing |
| 0001 | 1 | Indirect addressing through scratch pad |
| 0010 | 2 | Indirect addressing through base page (Page 0) |
| 0011 | 3 | Page relative addressing (current page) |
| 0100 | 4 | Base page relative addressing |
| 0101 | 5 | Program counter relative addressing |
| 0110 | 6 | Immediate addressing (2-word instruction) |
| 0111 | 7 | Direct index addressing (2-word instruction) |
| 1000 | 8 | Indirect indexed addressing |
| 1001 | 9 | Indexed indirect addressing |
| 1111 | F | Nonmemory reference instruction—A field of the instruction is |

Table 5-2 THE O-FIELD CODES FOR THE GEMINI-A INSTRUCTIONS

| Binary | HEX | Instruction |
|--------|-----|--|
| 0001 | 1 | Store, (ACC) → MEM |
| 0010 | 2 | Load, (MEM) → ACC and add (MEM) + (ACC) → ACC |
| 0011 | 3 | Load, (MEM) → ACC and subtract (ACC) - (MEM) → ACC |
| 0100 | 4 | Clear ACC |
| 0101 | 5 | Load index register (if the M code is the immediate address mode second word of that instruction will be loaded into the index register) |
| 0110 | 6 | Load scratch pad immediately. The address of the scratch-pad register will be given in the A field of the instruction, and the operand to be loaded will be in the second word of the instruction. |
| 0111 | 7 | JUMP, unconditional |